

ASSEMBLY-Assignment


Paluchuri Jyothsna (FWC22059)

Abstract—Design a sequential circuit modulo 5 counter


I. COMPONENTS NEEDED

| Component | Value | Quantity |
|-----------------------|--------------|----------|
| Arduino | Uno | 1 |
| Resistor | 220ohm | 1 |
| Bread board | - | 1 |
| Jumper wires | M-M | 20 |
| Seven segment Display | Common Anode | 1 |
| Decoder | 7447 | 1 |
| Flip Flop | 7474 | 2 |


II. 7447 IC PIN DIAGRAM

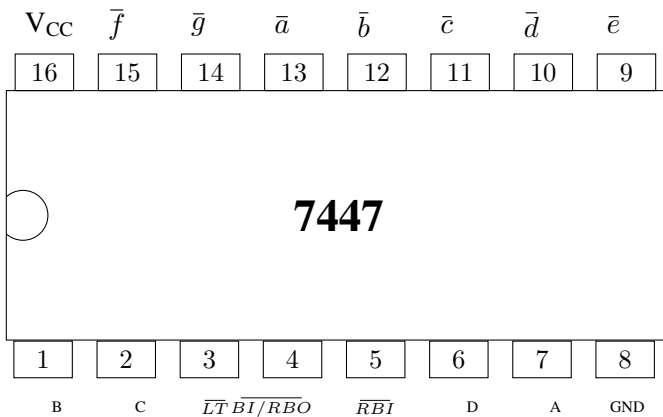

IV. SEVEN SEGMENT DISPLAY PINOUT

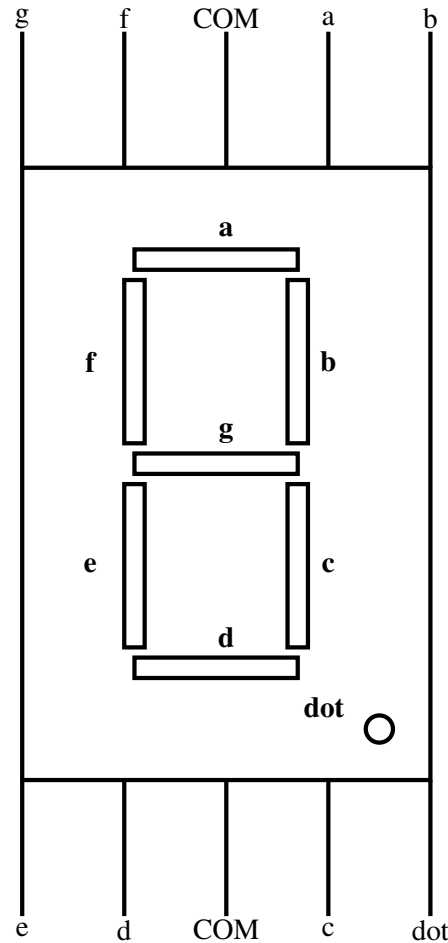

III. 7474 IC PIN DIAGRAM

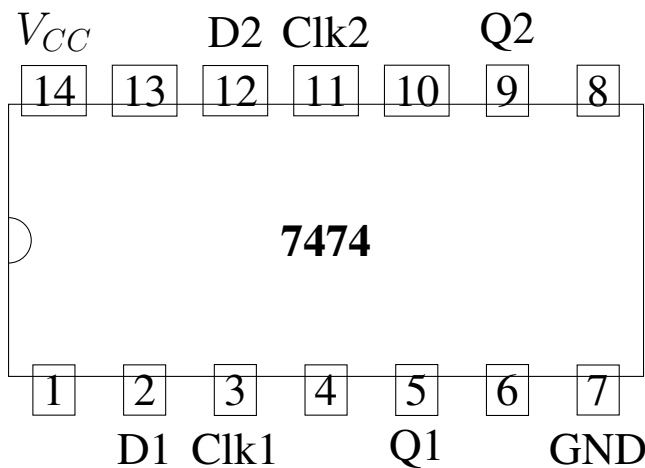

V. 7447 IC AND DISPLAY CONNECTION

| 7447 IC | Display |
|---------|---------|
| 13 | a |
| 12 | b |
| 11 | c |
| 10 | d |
| 9 | e |
| 15 | f |

Step 1: Make the connection of Seven Segment Display and 7447 according to the above table.


Step 2: Connect COM pin of 7 Segment display to 5v of Arduino Via 220 Ohm Resistor (else the display will damage) and Dot pin of display to GND pin of Arduino.

VI. CONECTION TABLE

| | INPUT | | | | OUTPUT | | | | CLOCK | 5V | | | | |
|---------|-------|----|----|----|--------|----|----|----|-------|------|----|---|----|----|
| | W | X | Y | Z | A | B | C | D | | | | | | |
| Arduino | D6 | D7 | D8 | D9 | D2 | D3 | D4 | D5 | D13 | | | | | |
| 7474 | 5 | 9 | | | 2 | 12 | | | CLK1 | CLK2 | 1 | 4 | 10 | 13 |
| 7474 | | | 5 | 9 | | | 2 | 12 | CLK1 | CLK2 | 1 | 4 | 10 | 13 |
| 7447 | | | | | 7 | 1 | 2 | 6 | | | 16 | | | |

Step 3: Make the connections of 7447 ,7474 and Arduino Board as per the above table.

VII. BLOCK DIAGRAM

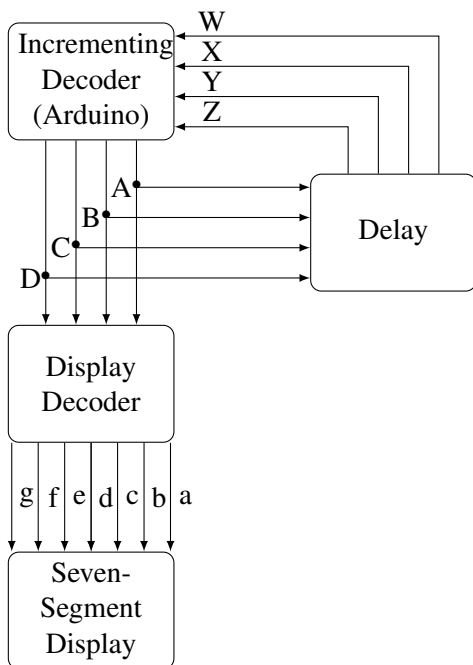

Step 4: Verify the Connections according to the Block diagram shown above

Step 5: After making all the connections Connect the Arduino Board to PC/Laptop Via USB cable.

Step 6: Download the code from the link below and upload into the Arduino.

<https://github.com/jyothsna777/jyothsna-fwc.git>

Step 7: Go on Geany and build and run the code

Step 8: Now verify the output in the 7 Seven Segment Display