

# IDE-Assignment


Paluchuri Jyothsna (FWC22059)

**Abstract**—Design a sequential circuit modulo 5 counter


## I. COMPONENTS NEEDED

Component	Value	Quantity
Arduino	Uno	1
Resistor	220ohm	1
Bread board	-	1
Jumper wires	M-M	20
Seven segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2


## II. 7447 IC PIN DIAGRAM

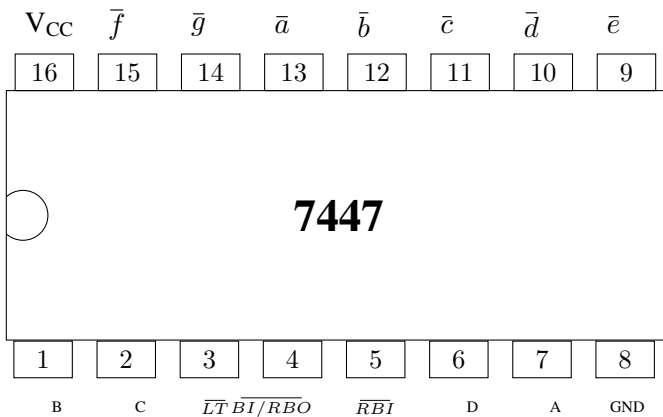

## III. 7474 IC PIN DIAGRAM

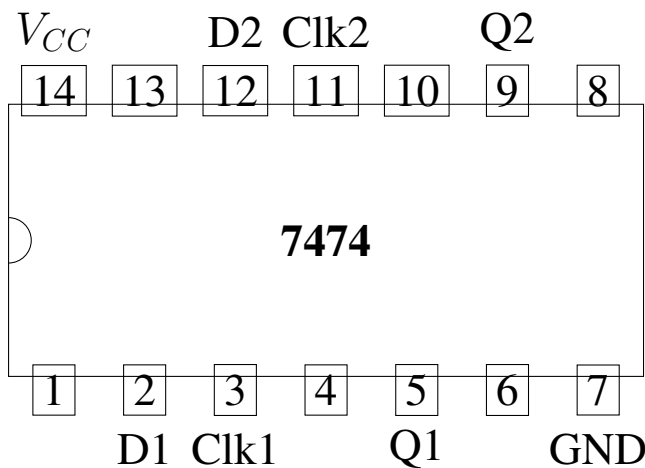

## IV. SEVEN SEGMENT DISPLAY PINOUT

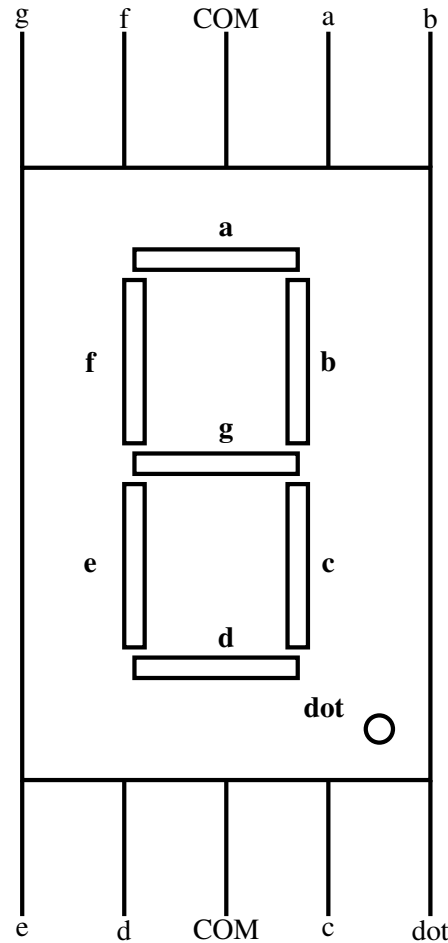

## V. 7447 IC AND DISPLAY CONNECTION

7447 IC	Display
13	a
12	b
11	c
10	d
9	e
15	f

**Step 1:** Make the connection of Seven Segment Display and 7447 according to the above table.


**Step 2:** Connect COM pin of 7 Segment display to 5v of Arduino Via 220 Ohm Resistor (else the display will damage) and Dot pin of display to GND pin of Arduino.

## VI. CONECTION TABLE

	INPUT				OUTPUT				CLOCK	5V				
	W	X	Y	Z	A	B	C	D						
Arduino	D6	D7	D8	D9	D2	D3	D4	D5	D13					
7474	5	9			2	12			CLK1	CLK2	1	4	10	13
7474			5	9			2	12	CLK1	CLK2	1	4	10	13
7447					7	1	2	6			16			

**Step 3:** Make the connections of 7447 ,7474 and Arduino Board as per the above table.

## VII. BLOCK DIAGRAM

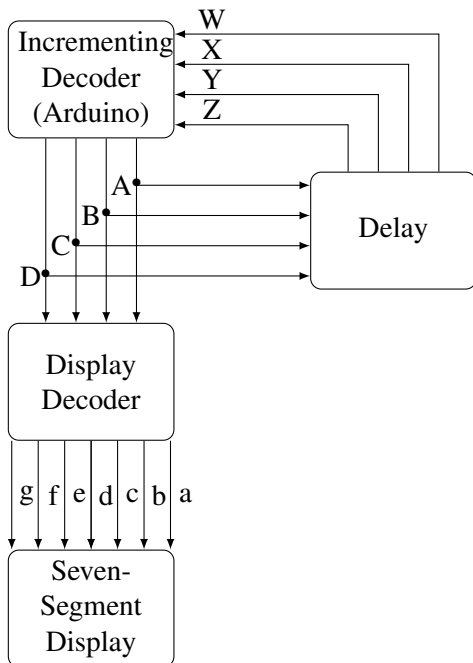

**Step 4:** Verify the Connections according to the Block diagram shown above

**Step 5:** After making all the connections Connect the Arduino Board to PC/Laptop Via USB cable.

**Step 6:** Download the code from the link below and upload into the Arduino.

<https://github.com/jyothsna777/jyothsna-fwc.git>

**Step 7:** Go to your working directory and execute the commands:

```
pio run
```

```
pio run -t upload
```

**Step 8:** Now verify the output in the 7 Seven Segment Display